



NATIONAL INSTITUTE OF TECHNOLOGY TIRUCHIRAPPALLI  
Cycle Test 1 – JULY, 2023 SESSION

Department	: Department of Computer Science and Engineering	
Date & Time of CT-I	: 07/09/2023 11:00 am to 12:00 pm	Venue: CSED
Sub Code & Title	: CSPC33 Digital Systems Design	Max. Marks: 20
Faculty Name	: R. Leela Velusamy	

Note to Student: Detailed answer is expected

Answer all questions

- ① What is the range of decimal value represented by a 16-bit binary number denoted as a) sign-magnitude form, b) unsigned form c) twos complement form? (3)
- ② Find the 16's complement of the number BCD3F. (1)
- ③ a) Analyze the circuit given in Figure 1 and derive the Boolean function for the output X (2)  
b) Rewrite the Boolean function in sum of minterms and product of Maxterms. (3)  
c) Implement the function after **simplification** using two level NAND – AND gates. (2 + 2)
4. Consider a four bit adder with carry lookahead. Derive the Boolean expression for the carry bits  $C_1$ ,  $C_2$ , and  $C_3$  in terms of carry generate  $G_i$  and carry propagate  $P_i$ . (3)
- ⑤ Draw a four-to-one multiplexer with an enable input and the corresponding truth table. (4)

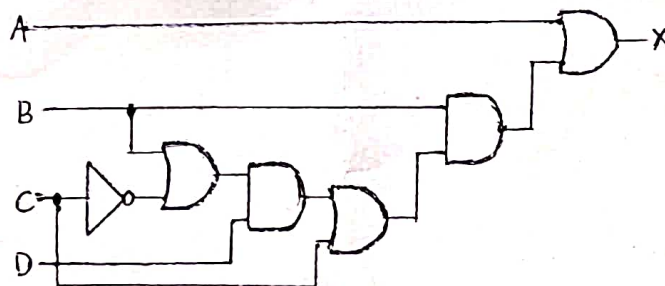


Figure 1

\*\*\*\*\*Best Wishes\*\*\*\*\*